



UGC-NET

Paper - 2

NATIONAL TESTING AGENCY (NTA)

ELECTRONIC SCIENCE

Paper 2 – Volume 2




Index

Unit – 3 (1)

1. Network Theory Ace	1
2. Thevenin theorem	23
3. Norton's Theorem	24
4. Maximum Power Transfer Theorem	40
5. Steady State AC Circuit Analysis	49
6. Capacitor	54
7. RMS Value /True/ Effective Value	65
8. Source transformation Technique	84
9. Maximum Power Transfer Theorem	88
10. Duals & Duality	105
11. Network topology or Graph Theory	109
12. Electrical Resonance	135
13. Electrical Transients	136
14. Network Theorems in Dc	198
15. Filters	217

Unit – 3 (1)


Network Theory Ace

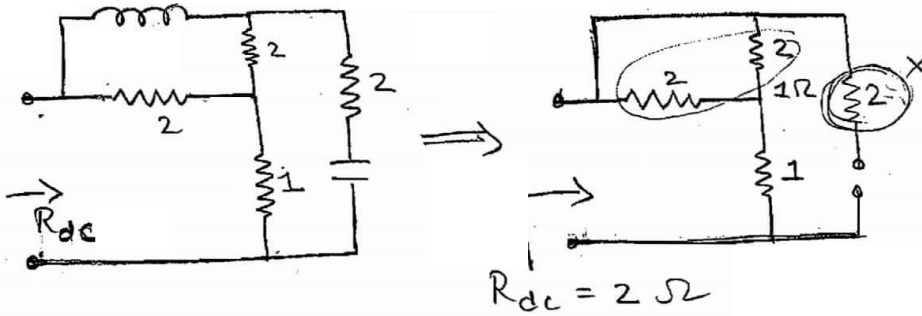



Methods of Analysis :

- Mesh Analysis = KVL + Ohms' Law
[I ↑ V ↓]
- Nodal Analysis = KCL + Ohms' Law
[V ↑ I ↓]

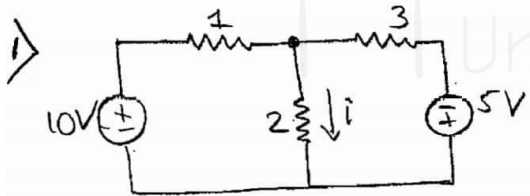In nodal analysis, we can eliminate the use of simple nodes, if not required.




Find i using mesh & nodal analysis

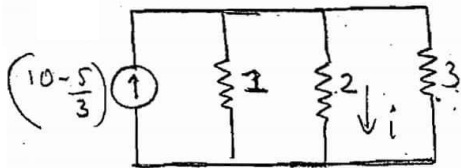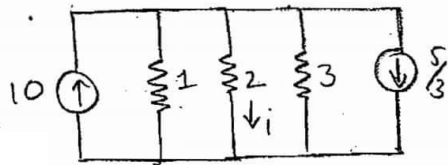

$$i = \left(10 - \frac{5}{3}\right) \left[\frac{3}{2+3+6} \right]$$
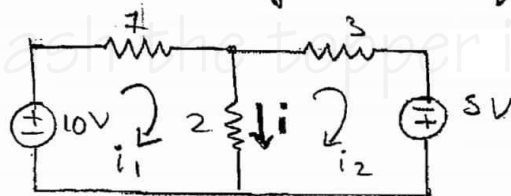
$$= \frac{25}{3} \times \frac{3}{11} = \frac{25}{11} A$$



Mesh Analysis

$$\textcircled{1} \quad 10 - 3i_1 + 2i_2 = 0$$

$$\therefore 3i_1 - 2i_2 = 10$$

$$\textcircled{2} \quad 5 - 5i_2 + 2i_1 = 0$$

$$\& 2i_1 - 5i_2 = -5$$


From $\textcircled{1}$ & $\textcircled{2}$ -

$$i_1 = \frac{60}{11} \quad i_2 = \frac{35}{11}$$

Now,

$$i = i_1 - i_2$$

$$= \frac{25}{11} A$$

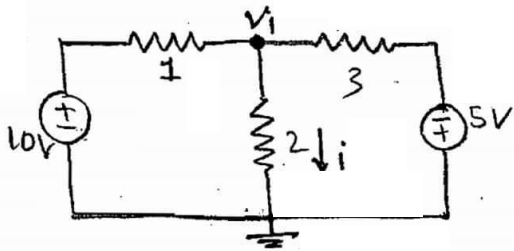

Nodal Analysis


$$\frac{V_1 - 10}{1} + \frac{V_1}{2} + \frac{V_1 - 5}{3} = 0$$

$$6V_1 - 60 + 3V_1 + 2V_1 - 10 = 0$$


$$V_1 = \frac{50}{11} \text{ V}$$

Now,
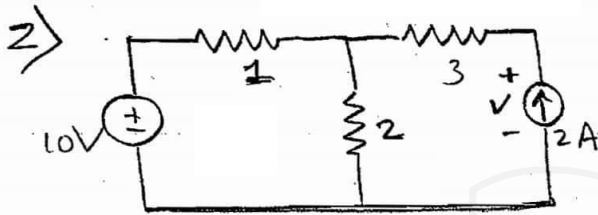
$$i = \frac{V_1}{2} = \frac{25}{11} \text{ A}$$



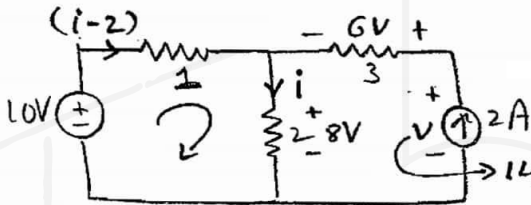
Find power delivered by current source using mesh & nodal



$$-10 + i - 2 + 2i = 0$$

$$i = 4 \text{ A}$$
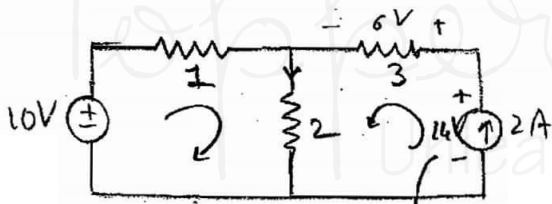
$$\therefore P_{deliv.} = + 2 \times 14 = 28 \text{ W}$$




$$-10 + i_1 + 2(i_1 - i_2) = 0$$

$$3i_1 - 2i_2 = 10 \quad \text{--- (1)}$$

$$\text{By comparison: } i_2 = -2 \quad \text{--- (2)}$$

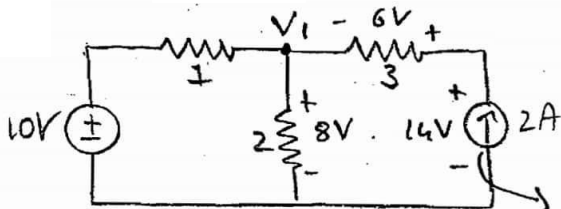
$$P_{del} = 28 \text{ W} \therefore 3i_1 = 6 \Rightarrow i_1 = 2$$




$$\frac{V_1 - 10}{1} + \frac{V_1}{2} - 2 = 0$$

$$\therefore V_1 = 8 \text{ V}$$

$$P_{del} = 28 \text{ W}$$

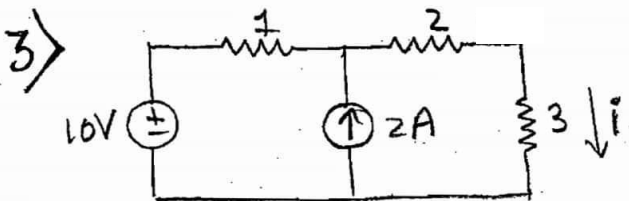


Find i using mesh & nodal analysis

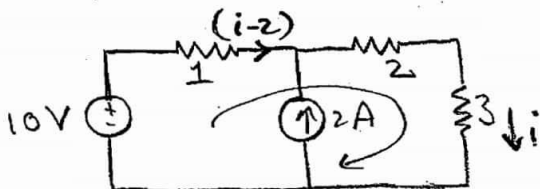

$$-10 - i - 2 + 5i = 0$$

$$i = 2$$

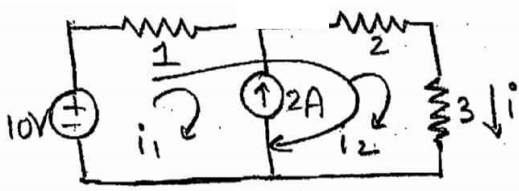

Here $i_2 = i$

$$10 - i_1 - 5i = 0$$


$$i_1 + 5i = 10$$

$$\therefore 6i = 12 \Rightarrow \boxed{i = 2 \text{ A}}$$

Now,

$$i - i_1 = 2$$


$$i_1 = i - 2$$

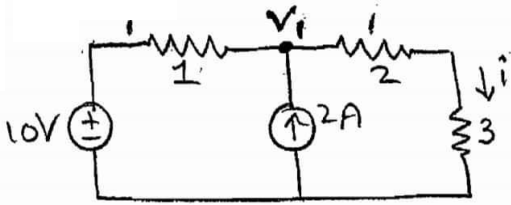




$$\frac{V_1 - 10}{1} = 2 + \frac{V_1}{5} = 0$$

$$6V_1 = 60 \Rightarrow V_1 = 10 \text{ V}$$
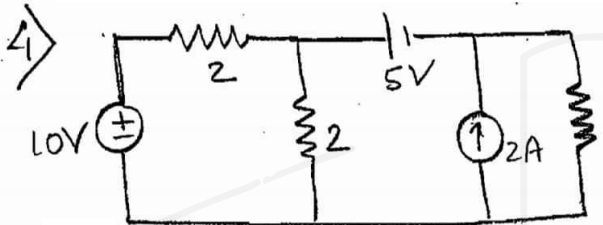
$$i = \frac{V_1}{5} = \frac{10}{5} = 2 \text{ A}$$



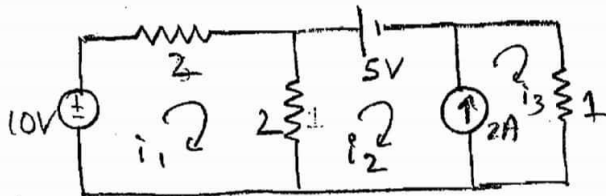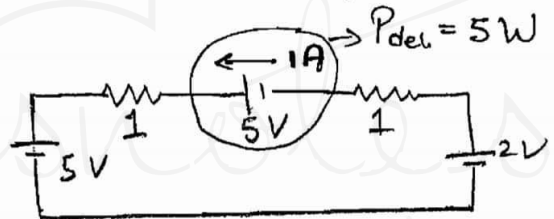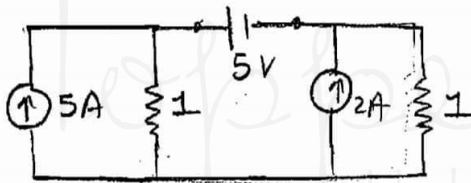Find the power delivered by 5V source using mesh and nodal analysis.



$$-10 + 2i_1 + 2(i_1 - i_2) = 0$$

$$2i_1 - i_2 = 5 \quad \text{--- (1)}$$

$$2(i_2 - i_1) + 5 + i_3 = 0$$

$$-2i_1 + 2i_2 + i_3 = 5 \quad \text{--- (2)}$$


$$-i_2 + i_3 = 2 \quad \text{--- (3)}$$

$$i_2 + i_3 = 0$$

$$2i_2 = -2$$

$$i_2 = -1$$
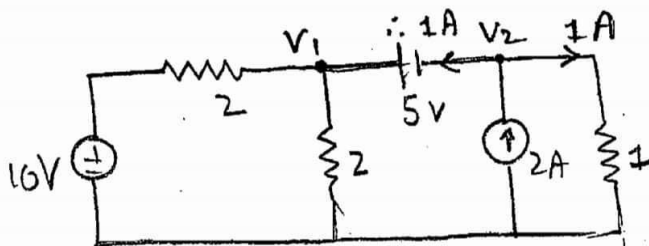
$$\Rightarrow \boxed{P_{del.} = 5 \text{ W}}$$



$$\frac{V_1 - 10}{2} + \frac{V_1}{2} - 2 + \frac{V_2}{1} = 0$$


$$V_1 + V_2 = 7 \quad \text{--- (1)}$$

$$V_1 - V_2 = 5 \quad \text{--- (2)}$$

$$\therefore V_1 = 6 \text{ V}$$

$$V_2 = 1 \text{ V}$$
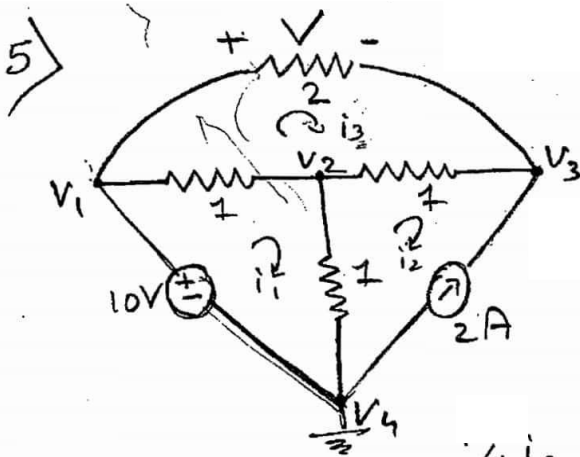
$$\therefore P_{deliv.} = 5 \times 1 = 5 \text{ W.}$$



Find V using mesh & nodal analysis

MESH :-

$$10 - 2i_1 + i_3 + i_2 = 0 \quad \text{--- (1)}$$

$$i_2 = -2 \quad \text{--- (2)}$$

$$4i_3 - i_1 - i_2 = 0 \quad \text{--- (3)}$$

$$\therefore -2i_1 + i_3 + 8 = 0$$

$$\& -i_1 + 4i_3 + 2 = 0$$

$$\therefore V = 2 \left(\frac{8}{7} \right) = \boxed{\frac{8}{7} \text{ V}}$$

$$\Rightarrow 4i_3 - 2i_1 = -8$$

$$\frac{-8i_3 + 2i_1 = +24}{-7i_3 - 7 = -104}$$

$$-7i_3 - 7 = -104$$

$$i_3 = \frac{79}{7} = \frac{4}{7}$$

NODAL :-

$$V_1 = 10 \text{ V} \quad \text{--- (1)}$$

$$\frac{V_2 - 10}{1} + \frac{V_2 - V_3}{1} + \frac{V_2}{1} = 0$$

$$\therefore 3V_2 - V_3 = 10 \quad \text{--- (2)}$$

$$\frac{V_3 - V_2}{1} + \frac{V_3 - 10}{2} - 2 = 0$$

$$\therefore 3V_3 - 2V_2 = 14 \quad \text{--- (3)}$$

From (2) & (3), ;

$$\therefore V = V_1 - V_3$$


$$= 10 - \frac{62}{7}$$

$$\boxed{V = \frac{8}{7} \text{ V}}$$

$$6V_2 - 2V_3 = 20$$

$$\frac{-6V_2 + 9V_3 = 42}{7V_3 = 62}$$

$$V_3 = \frac{62}{7}$$

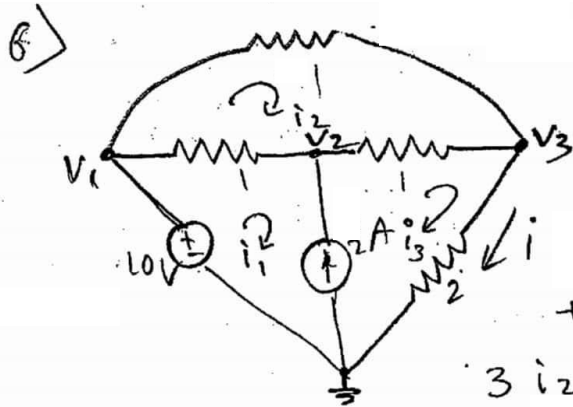

Find 'i' using mesh & nodal.

Mesh :-

$$+10 - i_1 \cdot i_3 - i_1 = 2 \quad \text{--- (1)}$$

$$3i_2 - i_1 - i_3 = 0 \quad \text{--- (2)}$$

$$10 - i_1 - 3i_3 + 2i_2 = 0 \quad \text{--- (3)}$$

Now, from (2) & (1); $3i_2 - i_3 + 2 - i_3 = 0$

$$3i_2 - 2i_3 = -2 \quad \text{--- (4)}$$

Now, from (1) & (3); $-i_3 + 2 - 3i_3 + 2i_2 = 10$

$$\therefore 2i_2 - 4i_3 = +8 \quad \text{--- (5)}$$

$$6i_2 - 2i_3 = -4$$

$$-6i_2 + 12i_3 = -24$$

$$\hline 8i_3 = -28$$

NODAL :- $V_1 = 10 \text{ V} \quad \text{--- (1)}$

$$\frac{V_2 + 10}{1} + \frac{V_2 - V_3}{1} - 2 = 0$$

$$2V_2 - V_3 = 12 \quad \text{--- (2)}$$


$$\frac{V_3 - 10}{1} + \frac{V_3 - V_2}{1} + \frac{V_3}{2} = 0$$

$$\therefore -2V_2 + 5V_3 = 20 \quad \text{--- (3)}$$

$$\therefore 4V_3 = 32$$

$$V_3 = 8 \text{ V}$$
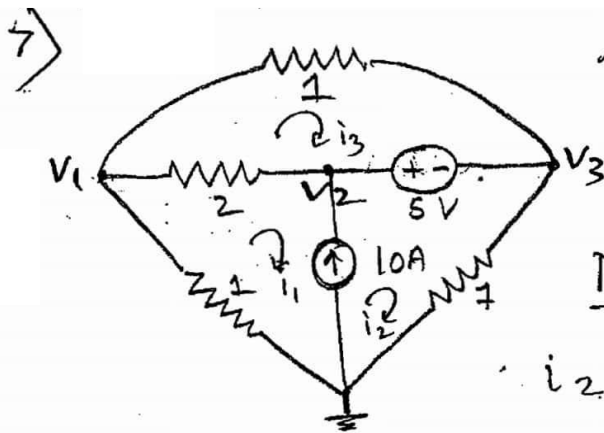
$$\Rightarrow i = \frac{8}{2} = \boxed{4 \text{ A}}$$



What is the power delivered by the voltage source?

Mesh :-

$$i_2 - i_1 = 10 \quad \text{--- (1)}$$

$$3i_1 + 2i_2 - 2i_3 = -5$$

$$\therefore 3(i_2 - 10) + 2i_2 - 2i_3 = -5$$

$$3i_2 - 30 + 2i_2 - 2i_3 = -5$$

$$\therefore 5i_2 - 2i_3 = 25 \quad \text{--- (2)}$$

$$3i_3 - 2i_1 = 5$$

$$3i_3 - 2(i_2 - 10) = 5$$

$$\therefore -2i_2 + 3i_3 = -25 \quad \text{--- (3)}$$

$$10i_2 - 6i_3 = 75$$

$$-4i_2 + 6i_3 = -30$$

$$\hline 8i_2 = 45$$

$$\therefore \boxed{i_2 = \frac{45}{8}}$$

$$i_3 = \frac{4\left(\frac{45}{8}\right) - 25}{2}$$

$$= \frac{45 - 50}{4} = -\frac{5}{4}$$

$$P_{del.} = -5 \times \left(\frac{45}{8} + \frac{5}{4}\right)$$

$$= \boxed{-\frac{275}{8} \text{ W}}$$

NODAL :-

$$\frac{V_1}{1} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{1} = 0$$

$$5V_1 - V_2 - 2V_3 = 0 \quad \text{--- (1)}$$

$$(V_2 - V_3) = 5 \quad \text{--- (2)}$$

$$\frac{V_2 - V_1}{2} - 10 + \frac{V_3}{1} + \frac{V_3 - V_1}{1} = 0$$

$$-3V_1 + V_2 + 4V_3 = 20 \quad \text{--- (3)}$$

From (1) & (2)

$$-7V_1 - V_2 = 20$$

From (2) & (3);


$$\frac{5V_1 - 3V_2 = -10}{16V_1 = 70}$$

$$V_2 = 7\left(\frac{35}{8}\right) - 20$$


$$\therefore V_1 = \frac{35}{8}$$

$$\therefore V_2 = \frac{85}{8}$$
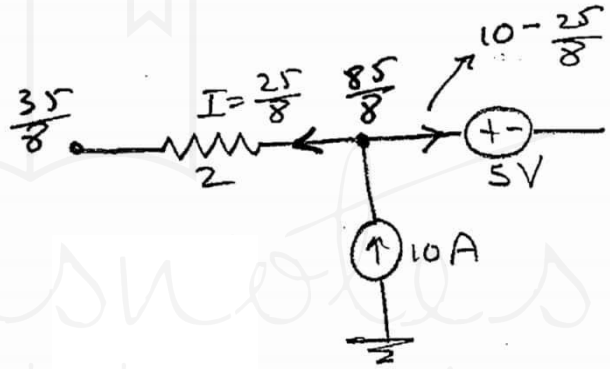
$$\begin{aligned} \therefore P_{\text{deliv}} &= -5\left(10 - \frac{25}{8}\right) \\ &= -\frac{275}{8} \text{ W} \end{aligned}$$



8

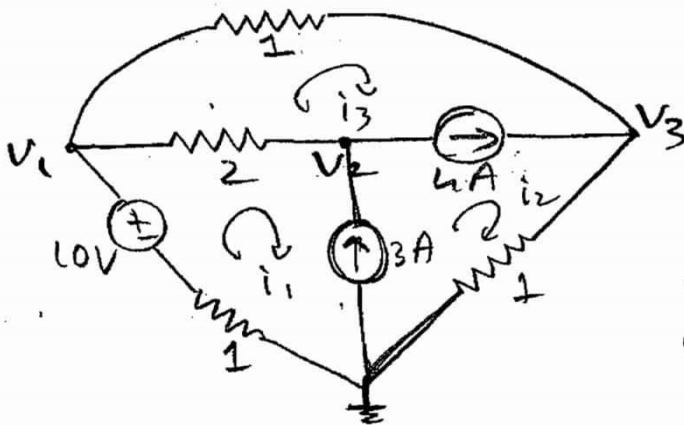

Find power delivered by 4A source using mesh & nodal.

MESH :-

$$i_1 + i_2 + i_3 = 10 \quad \text{--- (1)}$$

$$i_2 - i_1 = 3 \quad \text{--- (2)}$$

$$i_2 = 3 + i_1$$

$$i_2 - i_3 = 4 \quad \text{--- (3)}$$

$$3 + i_1 - i_3 = 4$$

$$\therefore i_3 = i_1 - 1$$

$$\therefore i_1 + 3 + i_1 + i_1 - 1 = 10$$

$$\therefore 3i_1 = 8 \Rightarrow i_1 = \frac{8}{3}$$

$$\therefore P_{\text{deliv.}} = 10 \times \frac{8}{3} = \boxed{\frac{80}{3} \text{ W}}$$

NODAL : —

$$\frac{V_1 - 10}{1} + \frac{V_1 - V_2}{2} + \frac{V_1 - V_3}{1} = 0$$

$$\therefore 5V_1 - V_2 - 2V_3 = 20 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{2} + 4 - 3 = 0$$

$$\therefore V_2 - V_1 = -2 \quad \text{--- (2)}$$

$$\frac{V_3}{1} - 4 + \frac{V_3 - V_1}{1} = 0$$

$$\therefore -V_1 + 2V_3 = 4 \quad \text{--- (3)}$$

From (1) & (2); $5V_1 - V_1 + 2 - 2V_3 = 20$

$$\therefore 4V_1 - 2V_3 = \frac{18}{1} \quad \text{--- (4)}$$

$$\therefore V_3 = \frac{4 + \frac{22}{3}}{2}$$


$$\frac{-V_1 + 2V_3 = 4}{3V_1} = \frac{4}{22}$$


$$\therefore V_3 = \frac{34}{6} \text{ V}$$

$$\therefore \boxed{V_1 = \frac{22}{3} \text{ V}}$$

Now,
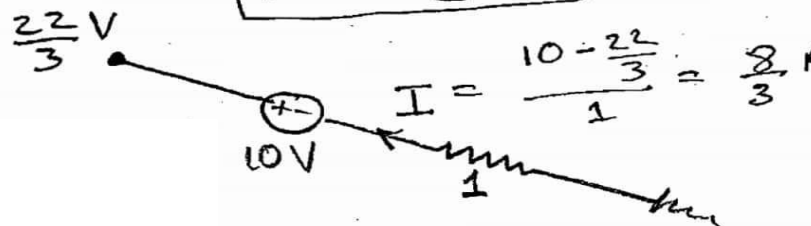
$$P_{\text{deliv.}} = 10 \times \frac{8}{3} = \frac{80}{3} \text{ W}$$



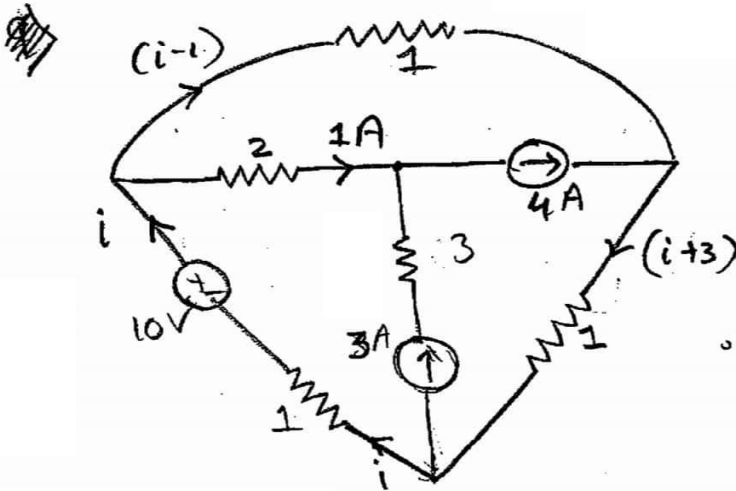


$$i - 10 + i - 1 + i + 3 = 0$$

$$3i = 8$$

$$i = \frac{8}{3}$$
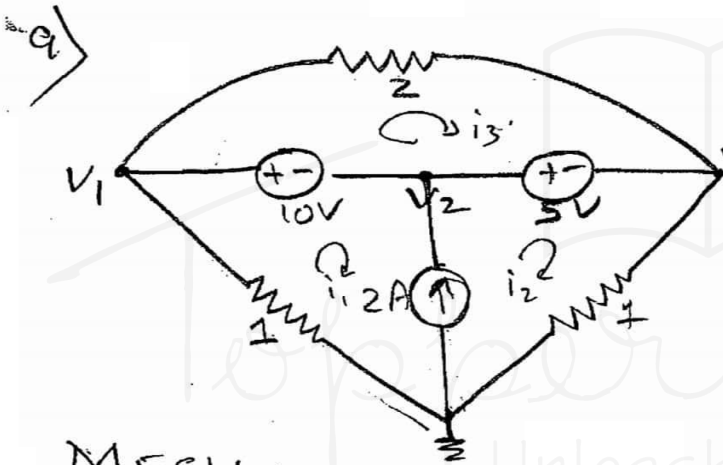
$$\therefore P_{\text{deliv.}} = 10 \times \frac{8}{3} = \frac{80}{3} \text{ W}$$



Find the power delivered by the current source using mesh & nodal.

MESH :-

$$i_1 + 1i_2 + 2i_3 = 0 \quad \text{--- (1) X}$$

$$2i_3 = 15 \Rightarrow \boxed{i_3 = \frac{15}{2}} \quad \text{--- (2)}$$


$$i_1 + i_2 = -15 \quad \text{--- (3)}$$

$$-i_1 + i_2 = 2 \quad \text{--- (4)}$$

$$\boxed{i_2 = -\frac{13}{2}}$$

$$i_1 = -\frac{17}{2}$$
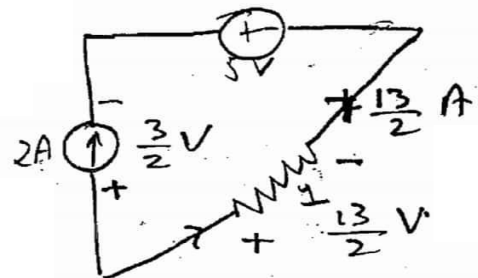
$$\therefore P_{\text{delivered}} = -2 \times \frac{3}{2} = \boxed{-3 \text{ W}}$$



NODAL :-

$$\frac{V_1}{1} + \frac{V_1 - V_3}{2} \rightarrow 2 + \frac{V_3}{1} + \frac{V_3 - V_1}{2} = 0$$

$$\therefore 3V_1 - V_3 = 4 \quad \text{--- (1)}$$

$$\therefore V_1 + V_3 = 2 \quad \text{--- (2)}$$

$$V_1 - V_2 = 10 \quad \text{--- (3)}$$

$$V_2 - V_3 = 5 \quad \text{--- (4)}$$

$$\Rightarrow V_2 + V_1 = 7$$


$$\therefore 2V_1 = 17$$

$$V_1 = \frac{17}{2}$$

$$V_2 = \frac{17}{2} - 10$$

$$V_2 = -\frac{3}{2} \text{ V}$$
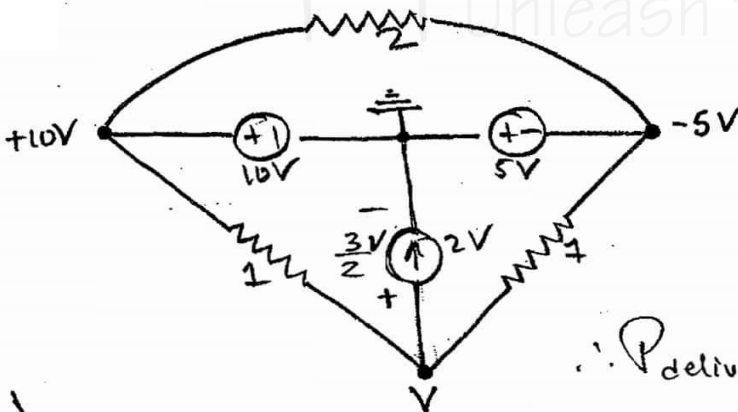
$$P_{\text{delivered}} = 2 \times \left(-\frac{3}{2}\right) = -3 \text{ W}$$




$$\frac{V-10}{1} + \frac{V+5}{1} + 2 = 0$$

$$\therefore 2V = 3$$

$$V = \frac{3}{2} \text{ V}$$

$$\therefore P_{\text{deliv.}} = -\frac{3}{2} \times 2 = -3 \text{ W}$$

10)

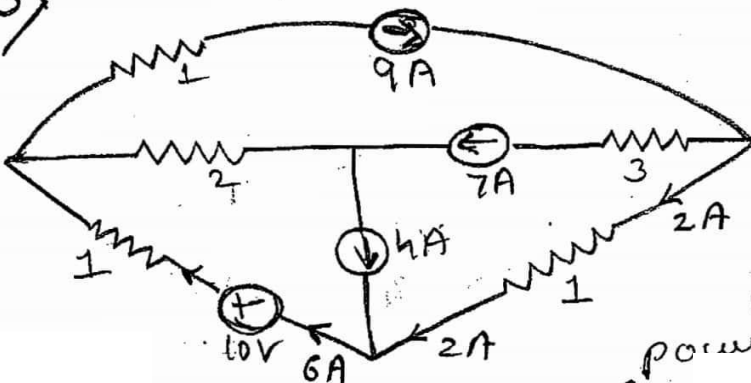

Just write mesh & nodal eqⁿ governing the circuit & determine power delivered by vltg source by inspection.

MESH :-

$$i_1 - i_2 = 4 \quad \text{--- (1)} \qquad i_3 = 9 \text{ A} \quad \text{--- (2)}$$

$$i_3 - i_2 = 7 \quad \text{--- (3)} \Rightarrow i_2 = 2 \text{ A}$$

$$\therefore i_1 = 6 \text{ A}$$

NODAL :-

$$\frac{V_1 - 10}{1} + \frac{V_1 - V_2}{2} + 9 = 0 \quad \text{--- (1)}$$


$$\therefore \frac{V_2 - V_1}{2} + 4 - 7 = 0 \quad \text{--- (2)}$$

$$\frac{V_3}{1} + 7 - 9 = 0 \quad \text{--- (3)}$$

Now,

$$P_{\text{delivered}} = 10 \times 6 = \boxed{60 \text{ W}}$$

11)

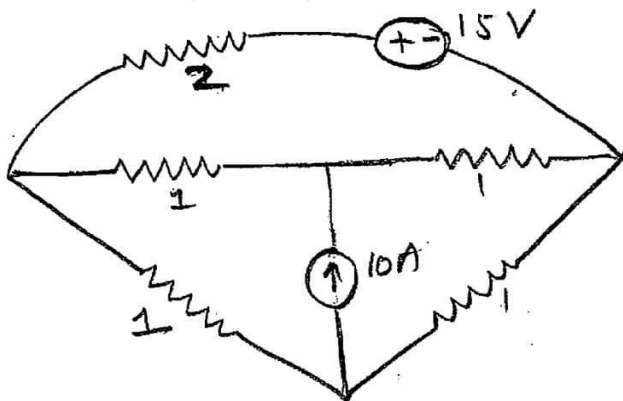

What is the power delivered by vltg source using mesh & nodal.

MESH :-

$$i_2 - i_1 = 10 \quad \text{--- (1)}$$

$$i_3 - i_1 - i_2 = -15 \quad \text{--- (2)} \Rightarrow i_1 + i_2 = i_3 + 15$$

$$i_1 + i_2 + 2i_3 = -15 \quad \text{--- (3)} \Rightarrow 2i_3 + 15 + 2i_3 = -15$$

$$P_{\text{delivered}} = +15 \times \frac{10}{2} = +\frac{150}{2} \text{ W} \qquad \therefore i_3 = \boxed{-5 \text{ A}}$$

NODAL: —

$$\frac{V_1}{1} + \frac{V_1 - V_2}{1} + \frac{V_1 - 15 - V_3}{2} = 0$$

$$\therefore 5V_1 - 2V_2 - V_3 = 15 \quad \text{--- (1)}$$

$$\frac{V_2 - V_1}{1} + \frac{V_2 - V_3}{1} - 10 = 0$$

$$\therefore -V_1 + 2V_2 - V_3 = 10 \quad \text{--- (2)}$$

$$\frac{V_3}{1} + \frac{V_3 - V_2}{1} + \frac{V_3 + 15 - V_1}{2} = 0$$

$$\therefore -V_1 - 2V_2 + 5V_3 = -15 \quad \text{--- (3)}$$

From (1) & (2); $4V_1 - 2V_3 = 25$

From (2) & (3); $\frac{-2V_1 + 4V_3}{4} = \frac{-5}{10}$

$$6V_3 = 15$$

$$V_1 = \frac{25 + \frac{15}{3}}{4}$$

$$V_3 = \frac{15}{6} \text{ V} = \frac{5}{2} \text{ V}$$


$$= \frac{90}{12} = \frac{15}{2} \text{ V}$$


$$\therefore I = \frac{V_3 + 15 - V_1}{2} = \frac{\frac{5}{2} + 15 - \frac{15}{2}}{2}$$

$$= \frac{20}{4} = 5 \text{ A}$$

$$\therefore P_{\text{delivered}} = 15 \times 5$$

$= 75 \text{ W}$

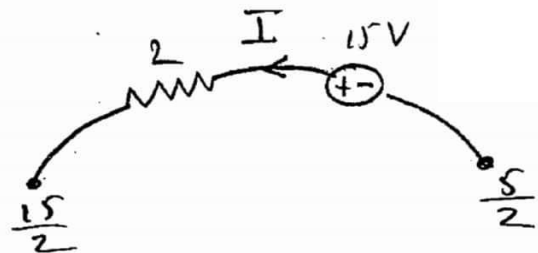

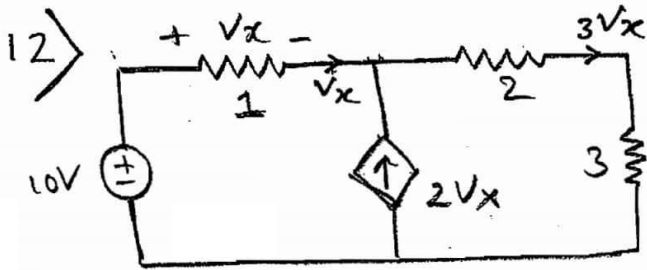

Find V_x using mesh & nodal

KVL $-10 + V_x + 15V_x = 0$

$\therefore \boxed{V_x = \frac{5}{8} V}$

MESH :-

$i_1 + 5i_2 = 10$ — (1)

$-i_1 + i_2 = 2V_x$ — (2)

$\therefore -3i_1 + i_2 = 0$ — (4)

Link equation :-

$V_x = i_1$ — (3)

From (1) & (4);

$$\begin{array}{r} 3i_1 + 15i_2 = 30 \\ -3i_1 + i_2 = 0 \\ \hline 16i_2 = 30 \\ i_2 = 2 \text{ A} \end{array}$$

$\therefore i_1 = \frac{5}{8} V$

$\therefore V_x = \frac{5}{8} V$

NODAL :-

$\frac{V_1 - 10}{1} - 2V_x + \frac{V_1}{5} = 0$


$5V_1 - 50 - 10V_x + V_1 = 0$

$6V_1 - 10V_x = 50$

$3V_1 - 5V_x = 25$ — (1)

$V_x = 10 - V_1$ — (2)

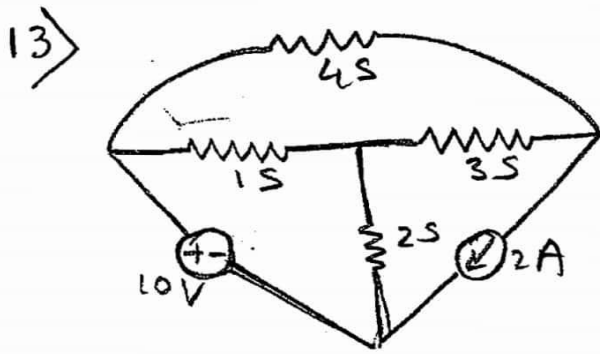$3(10 - V_x) - 5V_x = 25$
 $8V_x = 5$
 $V_x = \frac{5}{8} V$



MESH

$$-10 + \frac{(i_1 - i_3)}{1} + \frac{(i_1 - i_2)}{2} = 0 \quad \text{--- (1)}$$

$$\therefore i_2 = 2 \quad \text{--- (2)}$$

$$\frac{i_3}{4} + \frac{(i_3 - i_2)}{2} + \frac{(i_3 - i_1)}{1} = 0 \quad \text{--- (3)}$$

$$P_{3S} = \frac{|i_2 - i_3|^2}{3} = \quad \text{--- W}$$

NODAL :-


$$V_1 = 10 \quad \text{--- (1)}$$

$$1[V_2 - V_1] + 2V_2 + 3[V_2 - V_3] = 0 \quad \text{--- (2)}$$

$$+2 + 3(V_3 - V_2) + 4(V_3 - V_1) = 0 \quad \text{--- (3)}$$

$$P_{3S} = [V_2 - V_3]^2 \cdot 3 = \quad \text{--- W}$$


14)

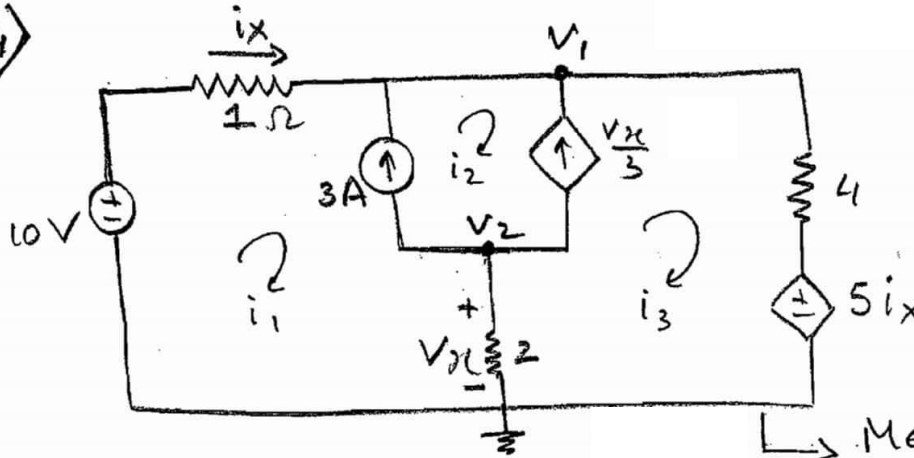

Write mesh & nodal equations governing the circuits.

Mesh = 3 + 2 = 5
 Nodal = 2 + 2 = 4

15)

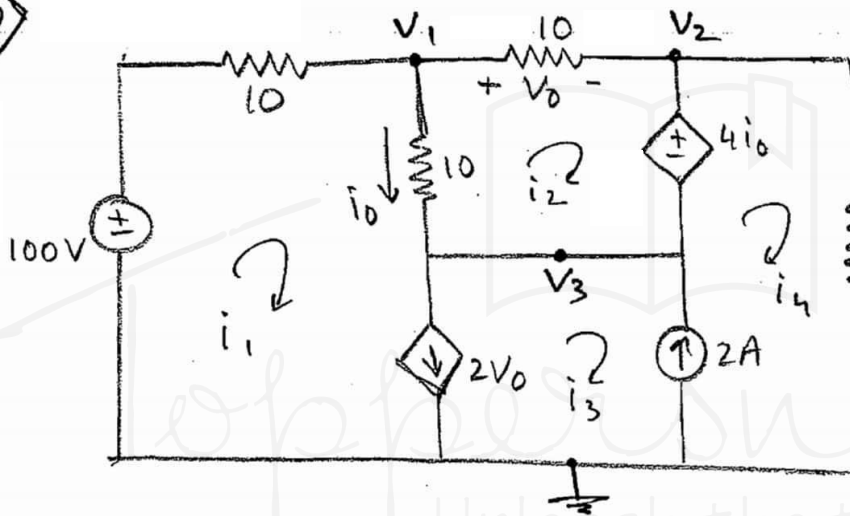

Mesh = 4 + 2 = 6
 Nodal = 3 + 2 = 5

14) MESH :-

$$10 - i_1 - 4i_3 - 5i_x = 0 \quad \text{--- (1)}$$

$$-i_1 + i_2 = 3 \quad \text{--- (2)}$$

$$-i_2 + i_3 = \frac{V_x}{2} \quad \text{--- (3)}$$

$$i_x = i_1 \quad \text{--- (4)}$$

$$V_x = (i_1 - i_3) \cdot 2 \quad \text{--- (5)}$$

NODAL :-

$$\frac{V_1 - 10}{1} + \frac{V_1 - 5i_x}{1} - 3 - \frac{V_x}{3} = 0 \quad \text{--- (1)}$$

$$\frac{V_2}{2} + 3 + \frac{V_x}{3} = 0 \quad \text{--- (2)}$$

$$V_x = V_2 \quad \text{--- (3)}$$

$$i_x = 10 - V_1 \quad \text{--- (4)}$$